

## UNIT 2

### Boolean Algebra

***This chapter includes:***

- 2.1 Introduction
- 2.2 Basic Operations
- 2.3 Boolean Expressions and Truth Tables
- 2.4 Basic Theorems
- 2.5 Commutative, Associative, Distributive and DeMorgan's Laws
- 2.6 Simplification Theorems
- 2.7 Multiplying Out and Factoring
- 2.8 Complementing Boolean Expressions

# Learning Objectives


- ❖ Understand the basic operations and laws of Boolean algebra.
- ❖ Relate these operations and laws to circuits composed of AND gates, OR gates, INVERTERS and switches.
- ❖ Prove any of these laws in switching algebra using a truth table.
- ❖ Apply these laws to the manipulation of algebraic expressions including: obtaining a sum of products or product of sums, simplifying an expression and/or finding the complement of an expression

# Introduction


- ❖ All switching devices we will use are two-state devices, so we will emphasize the case in which all variables assume only one of two values.
- ❖ Boolean variable X or Y will be used to represent input or output of switching circuit.
- ❖ Symbols "0" and "1" represent the two values any variable can take on. These represent states in a logic circuit, and do not have numeric value.
- ❖ Logic gate: 0 usually represents range of low voltages and 1 represents range of high voltages
- ❖ Switch circuit: 0 represents open switch and 1 represents closed
- ❖ 0 and 1 can be used to represent the two states in any binary valued system.
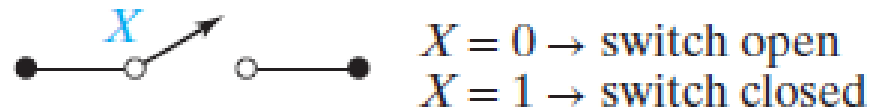
# Basic Operations

- ❖ The basic operations of Boolean (switching) algebra are called AND, OR, and complement (or inverse).
- ❖ To apply switching algebra to a switch circuit, each switch contact is labeled with a variable. See diagram below:



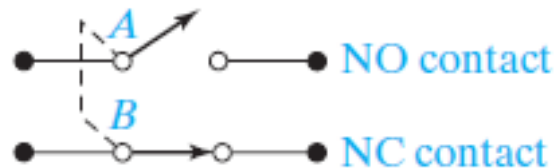- ❖ NC (normally closed) and NO (normally open) contacts are always in opposite states.




- ❖ If variable  $X$  is assigned to NO contact, then  $X'$  will be assigned for NC.

# Basic Operations
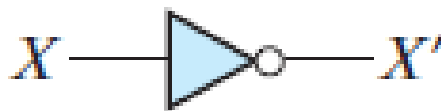
## Complementation/ Inversion:

- ❖ Prime (') denotes complementation.
- ❖  $0' = 1$  and  $1' = 0$
- ❖ For a switching variable,  $X$ :
  - ❖  $X' = 1$  if  $X = 0$  and  $X' = 0$  if  $X = 1$
- ❖ Complementation is also called inversion. An inverter is represented as shown below, where circle at the output denotes inversion:



# Basic Operations

## Series Switching Circuits/ AND Operation:

### Series:

- A) Truth table B) Logic gate diagram  
C) Switch circuit diagram

The operation defined by the table is called AND. It is written algebraically as  $C = A \cdot B$ . We will usually write  $AB$  instead of  $A \cdot B$ . The AND operation is also referred to as logical (or Boolean) multiplication.

A)

$A$	$B$	$C = A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1



C)



$C = 0 \rightarrow$  open circuit between terminals 1 and 2

$C = 1 \rightarrow$  closed circuit between terminals 1 and 2

# Basic Operations

## Parallel Switching Circuits/ OR Operation:



### Series:

- A) Truth table B) Logic gate diagram  
C) Switch circuit diagram

The operation defined by the table is called OR. It is written algebraically as  $C=A+B$ . The OR operation is also referred to as logical (or Boolean) addition.

A)

$A$	$B$	$C = A + B$
0	0	0
0	1	1
1	0	1
1	1	1

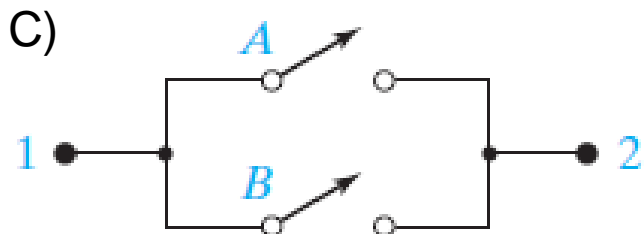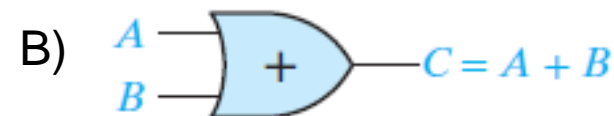

If switches A and B are connected in parallel, there is a closed circuit if either A or B, or both, are closed and an open circuit only if A and B are both open.



# Boolean Operations and Truth Tables

## Examples of Boolean Expressions and Corresponding Diagrams:



### Expressions

$$AB' + C \quad (2-1)$$

$$[A(C + D)]' + BE \quad (2-2)$$

Order of operations- Parentheses, Inversion, AND, OR

### Logic Diagrams

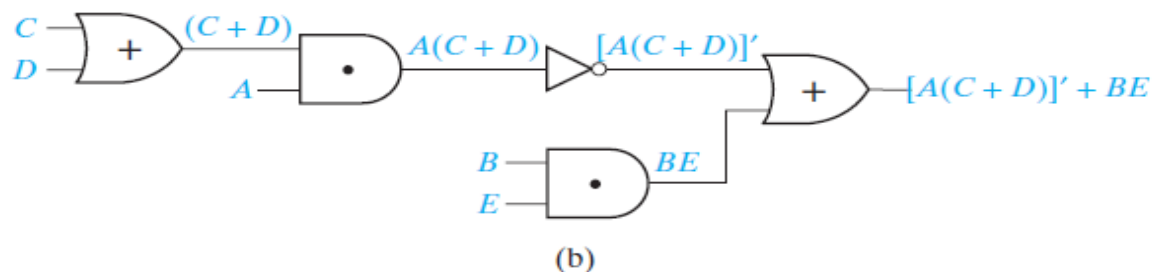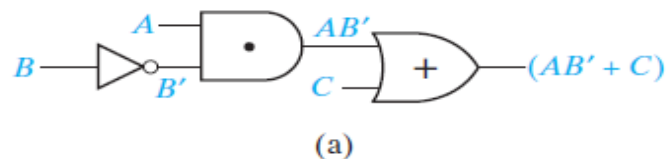

# Boolean Operations and Truth Tables


## Truth Tables:

A truth table specifies the values of a Boolean expression for every possible combination of values of the variables in the expression.

**FIGURE 2-2**

Two-Input Circuit  
and Truth Table

© Cengage Learning 2014

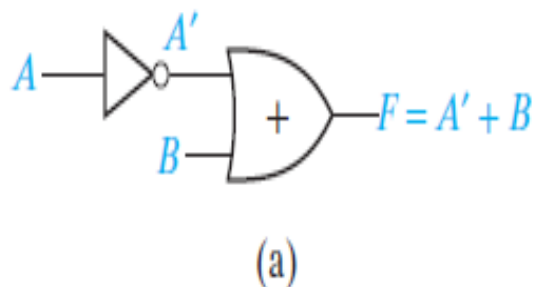

$A$	$B$	$A'$	$F = A' + B$
0	0	1	1
0	1	1	1
1	0	0	0
1	1	0	1

(b)

# Boolean Operations and Truth Tables

## Equal Boolean Expressions:

Two boolean expressions are said to be **equal** if they have the same value for every possible combination of the variables.

TABLE 2-1

© Cengage Learning 2014

A B C	B'	AB'	AB' + C	A + C	B' + C	(A + C)(B' + C)
0 0 0	1	0	0	0	1	0
0 0 1	1	0	1	1	1	1
0 1 0	0	0	0	0	0	0
0 1 1	0	0	1	1	1	1
1 0 0	1	1	1	1	1	1
1 0 1	1	1	1	1	1	1
1 1 0	0	0	0	1	0	0
1 1 1	0	0	1	1	1	1

$$AB' + C = (A + C)(B' + C) \quad (2-3)$$

An n-variable expression will have  $2^n$  rows in its truth table.

# Basic Theorems

## Single Variable Basic Theorems:

Operations with 0 and 1:

$$X + 0 = X \quad (2-4)$$

$$X \cdot 1 = X \quad (2-4D)$$

$$X + 1 = 1 \quad (2-5)$$

$$X \cdot 0 = 0 \quad (2-5D)$$

Idempotent laws:

$$X + X = X \quad (2-6)$$

$$X \cdot X = X \quad (2-6D)$$

Involution law:

$$(X')' = X \quad (2-7)$$

Laws of complementarity:

$$X + X' = 1 \quad (2-8)$$

$$X \cdot X' = 0 \quad (2-8D)$$

See book for switch circuit diagrams that illustrate these basic theorems (Roth-Kinney 7<sup>th</sup> edition, pg 42-43).

# Commutative, Associative, Distributive and DeMorgan's Laws

## Commutative and Associative Laws:

**Commutative:** Order in which variables are written does not affect result of applying AND and OR operations.

$$XY = YX \text{ and } X+Y = Y+X$$

**Associative:** Result of AND and OR operations is independent of which variables we associate together first.

$$(XY)Z = X(YZ) = XYZ$$

$$(X+Y)+Z = X+(Y+Z) = X+Y+Z$$

# Commutative, Associative, Distributive and DeMorgan's Laws

## **Distributive Law:**

The distributive law of boolean algebra is as follows:

$$X(Y+Z) = XY + XZ$$

Furthermore, a second distributive law is valid for Boolean algebra but not ordinary algebra:

$$X + YZ = (X + Y)(X + Z)$$

Proof of this second distributive law can be found on page 45.

# Commutative, Associative, Distributive and DeMorgan's Laws

## DeMorgan's Laws:

DeMorgan's Law is stated as follows:

$$(X+Y)' = X'Y'$$

$$(XY)' = X' + Y'$$

Truth table proof of DeMorgan's Laws is shown below:

$X$	$Y$	$X' Y'$	$X + Y$	$(X + Y)'$	$X' Y'$	$XY$	$(XY)'$	$X' + Y'$
0	0	1 1	0	1	1	0	1	1
0	1	1 0	1	0	0	0	1	1
1	0	0 1	1	0	0	0	1	1
1	1	0 0	1	0	0	1	0	0

# Commutative, Associative, Distributive and DeMorgan's Laws

## Laws of Boolean Algebra(Table 2-3):

Operations with 0 and 1:

$$1. X + 0 = X$$

$$2. X + 1 = 1$$

$$1D. X \cdot 1 = X$$

$$2D. X \cdot 0 = 0$$

Idempotent laws:

$$3. X + X = X$$

$$3D. X \cdot X = X$$

Involution law:

$$4. (X')' = X$$

Laws of complementarity:

$$5. X + X' = 1$$

$$5D. X \cdot X' = 0$$



# Commutative, Associative, Distributive and DeMorgan's Laws

## Laws of Boolean Algebra- (continued):

Commutative laws:

$$6. X + Y = Y + X$$

$$6D. XY = YX$$

Associative laws:

$$7. (X + Y) + Z = X + (Y + Z) \\ = X + Y + Z$$

$$7D. (XY)Z = X(YZ) = XYZ$$

Distributive laws:

$$8. X(Y + Z) = XY + XZ$$

$$8D. X + YZ = (X + Y)(X + Z)$$

DeMorgan's laws:

$$9. (X + Y)' = X'Y'$$

$$9D. (XY)' = X' + Y'$$

# Simplification Theorems

## Simplification theorems:

Theorems used to replace an expression with a simpler expression are called **simplification theorems**.

Uniting theorems:

$$1. XY + XY' = X$$

$$1D. (X + Y)(X + Y') = X$$

Absorption theorems:

$$2. X + XY = X$$

$$2D. X(X + Y) = X$$

Elimination theorems:

$$3. X + X'Y = X + Y$$

$$3D. X(X' + Y) = XY$$

Duality:

$$4. (X + Y + Z + \dots)^D = XYZ \dots$$

$$4D. (XYZ \dots)^D = X + Y + Z + \dots$$

Theorems for multiplying out and factoring:

$$5. (X + Y)(X' + Z) = XZ + X'Y$$

$$5D. XY + X'Z = (X + Z)(X' + Y)$$

Consensus theorems:

$$6. XY + YZ + X'Z = XY + X'Z$$

$$6D. (X + Y)(Y + Z)(X' + Z) = (X + Y)(X' + Z)$$

# Simplification Theorems

## Proof of Simplification Theorems:

- ❖ Using switching algebra, the theorems on the previous slide can be proven using truth tables.
- ❖ In general Boolean algebra, these theorems must be proven algebraically starting with basic theorems.

Proof of (2-15):  $XY + XY' = X(Y + Y') = X(1) = X$

Proof of (2-16):  $X + XY = X \cdot 1 + XY = X(1 + Y) = X \cdot 1 = X$

Proof of (2-17):  $X + X'Y = (X + X')(X + Y) = 1(X + Y) = X + Y$

Proof of (2-18):  $XY + X'Z + YZ = XY + X'Z + (1)YZ =$   
 $XY + X'Z + (X + X')YZ = XY + XYZ + X'Z + X'YZ =$   
 $XY + X'Z$  (using absorption twice)

- ❖ Using duality property, (2-15D)-(2-18D) can be proven

# Multiplying Out and Factoring

## Sum of Products:

An expression is said to be in *sum-of-products* (SOP) form when all products are the products of single variables. This form is the end result when an expression is fully multiplied out.

For example:

$$AB' + CD'E + AC'E'$$

$$ABC' + DEFG + H$$

# Multiplying Out and Factoring

## Product of Sums:

An expression is in *product-of-sums* (POS) form when all sums are the sums of single variables. It is usually easy to recognize a product-of-sums expression since it consists of a product of sum terms.

For example:

$$(A + B')(C + D' + E)(A + C' + E')$$

$$(A + B)(C + D + E)F$$

# Multiplying Out and Factoring

## Examples:

### Example 1

Factor  $A + B'CD$ . This is of the form  $X + YZ$  where  $X = A$ ,  $Y = B'$ , and  $Z = CD$ , so

$$A + B'CD = (X + Y)(X + Z) = (A + B')(A + CD)$$

$A + CD$  can be factored again using the second distributive law, so

$$A + B'CD = (A + B')(A + C)(A + D)$$

### Example 2

Factor  $AB' + C'D$ .

$$AB' + C'D = (AB' + C')(AB' + D) \quad \leftarrow \text{note how } X + YZ = (X + Y)(X + Z) \text{ was applied here}$$

$$= (A + C')(B' + C')(A + D)(B' + D) \quad \leftarrow \text{the second distributive law was applied again to each term}$$

# Complementing Boolean Expressions

## Using DeMorgan's Laws to find Inverse Expressions:

- ❖ The complement or inverse of any Boolean expression can be found using DeMorgan's Laws.
- ❖ DeMorgan's Laws for n-variable expressions:

$$(X_1 + X_2 + X_3 + \cdots + X_n)' = X_1' X_2' X_3' \cdots X_n' \quad (2-25)$$

$$(X_1 X_2 X_3 \cdots X_n)' = X_1' + X_2' + X_3' + \cdots + X_n' \quad (2-26)$$

For example, for  $n = 3$ ,

$$(X_1 + X_2 + X_3)' = (X_1 + X_2)' X_3' = X_1' X_2' X_3'$$

- ❖ The complement of the product is the sum of the complements.
- ❖ The complement of the sum is the product of the complements.

# Complementing Boolean Expressions

## Examples:

### Example 1

To find the complement of  $(A' + B)C'$ , first apply (2-13) and then (2-12).

$$[(A' + B)C']' = (A' + B)' + (C')' = AB' + C$$

### Example 2

$$\begin{aligned} [(AB' + C)D' + E]' &= [(AB' + C)D']'E' && \text{(by (2-12))} \\ &= [(AB' + C)' + D]E' && \text{(by (2-13))} \\ &= [(AB')'C' + D]E' && \text{(by (2-12))} \\ &= [(A' + B)C' + D]E' && \text{(by (2-13)) (2-27)} \end{aligned}$$

Note that in the final expressions, the complement operation is applied only to single variables.